



Faculty of Engineering  
ASU


## Term Project

### MultiStage BJT Audio Amplifier With Volume Control

ECE 131 : Electronic Engineering

1<sup>st</sup> year Electrical Engineering

Spring 2017

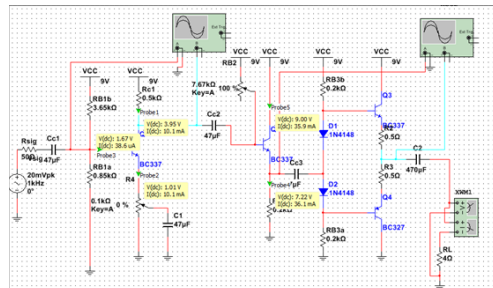

Submitted By:

Nada Ihab Ahmed Mohamed Abdelgawad

Submitted To:

Dr/Hesham Omran

2017/2018

Cairo, Egypt

## Table Of Contents

Page No.	Content
3	1.DC and Ac load line
4	2.Determination of components values
7	3.A table summarizing the component values
8	4.Simulation Results
10	5.Comparison between simulation & hand result
12	6.Prototype photograph
13	7.Maximum and Minimum Frequency
14	8. Power supply

## 1.Dc and Ac load lines


### DC Analysis:

Applying output KVL:

$$-V_{CC} + V_{CE} + I_E R_{E2} = 0$$

$$I_E = \frac{V_{CC} - V_{CE}}{R_{E2}} ; I_E \approx I_C ,$$
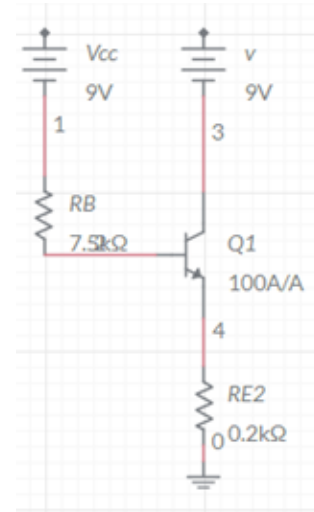
$$I_C = \frac{V_{CC} - V_{CE}}{R_{E2}} \Rightarrow \text{DC load line}$$




### AC Analysis:

Applying output KVL:

$$V_{CE} + I_E (R_{E2} // R_{in3}) = 0$$

$$I_E = \frac{-V_{CE}}{R_{E2} // R_{in3}} ; I_E \approx I_C ,$$
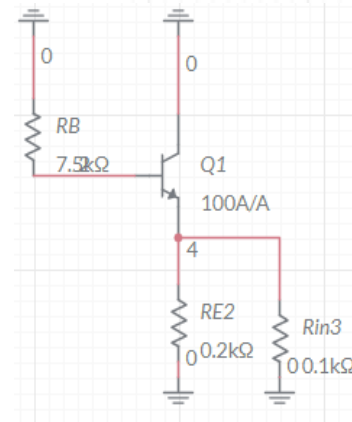
$$I_C = \frac{-V_{CE}}{R_{E2} // R_{in3}} \Rightarrow \text{AC load line.}$$




Get Vpk:

$$\text{Slope} = \frac{1}{R_{E2} // R_{in3}} = \frac{I_{CQ}}{V_{pk}}$$

$$V_{pk} = I_{CQ} \cdot (R_{E2} // R_{in3}) ; I_{CQ} = \frac{V_{E2}}{R_{E2}} ,$$

$$V_{pk} = \frac{V_{E2}}{R_{E2}} \cdot (R_{E2} // R_{in3})$$
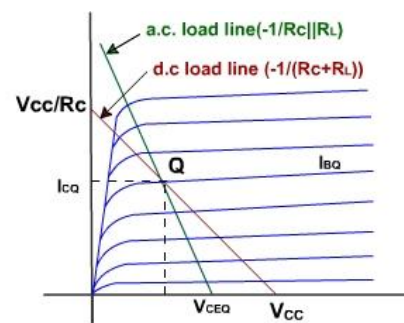
$$V_{pk} = V_{E2} \cdot \frac{R_{in3}}{R_{in3} + R_{E2}}$$



## 2 . Determination of components values

### Power Amplifier AB Class

#### DC Analysis:

Assume  $R_{in3}=0.1k\Omega$


Since  $R_{in3}=R_{B3a} // R_{B3b} // \beta R_L$

$\approx R_{B3a} // R_{B3b}$

Since this stage is symmetric :

$R_{B3a}=R_{B3b}=0.2k\Omega$

$A_{v3}=1$

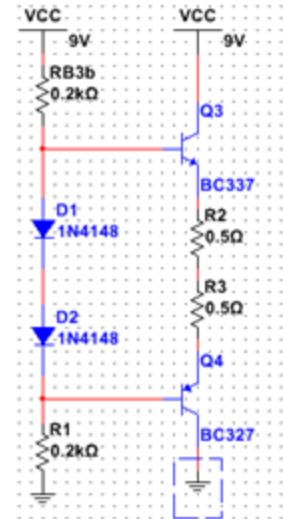

## Common Collector Analysis

### DC Analysis:

$$V_{pk} = V_{E2} = \frac{R_{in3}}{R_{in3} + R_{E2}}$$

$$2 = 6 \frac{0.1k}{R_{E2} + 0.1k} \Rightarrow R_{E2} = 0.2\Omega$$

$$I_{E2} = \frac{V_{E2}}{R_{E2}} = 30mA, I_{B2} = \frac{V_{E2}}{R_{E2}} = 0.297mA$$

Applying input KVL:


$$-9 + I_B R_{B2} + 0.7 + 6 = 0$$

$$R_{B2} = 7.67k\Omega$$

GET Small Signal Parameters:

$$g_m = \frac{I_C}{V_T} = \frac{I_C}{26m} = 1.15 S$$
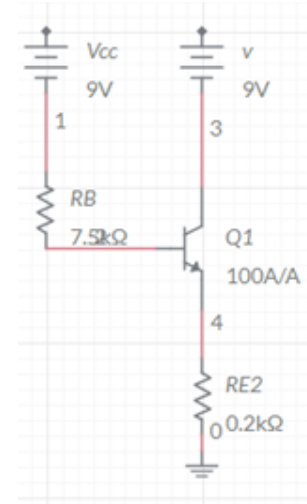
$$r_{\pi} = \frac{\beta}{g_m} = 86.9\Omega$$



### AC Analysis:

$$R_{in2} = \frac{V_{in}}{I_x} = \frac{V_{\pi} + \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) (R_{E2} // R_{in3})}{\frac{V_{\pi}}{r_{\pi}}}$$

$$= r_{\pi} (1 + (R_{E2} // R_{in3})) = 6.72k$$

$$R_{out2} = \frac{V_{out}}{I_x} = \frac{V_{\pi} + \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) (R_{E2} // R_{in3})}{\left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right)}$$


$$= \frac{1 + g_m (R_{E2} // R_{in3})}{g_m} = 99.58 \Omega$$

$$V_{in} = V_{\pi} + \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) (R_{E2} // R_{in3})$$

$$V_{out} = \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) (R_{E2} // R_{in3})$$

$$A_{v2} = \frac{V_{out}}{V_{in}} = \frac{\left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) (R_{E2} // R_{in3})}{V_{\pi} + \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) (R_{E2} // R_{in3})} =$$
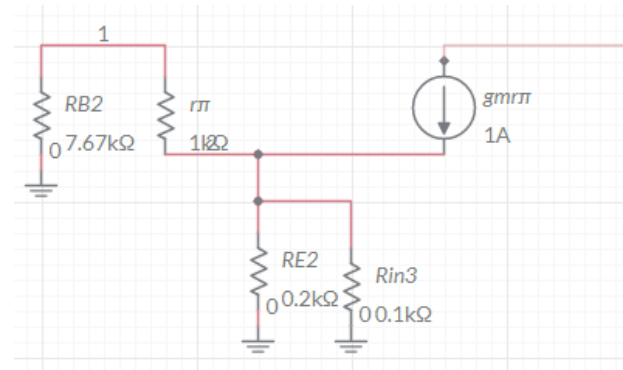
$$\frac{g_m (R_{E2} // R_{in3})}{1 + g_m (R_{E2} // R_{in3})} = 0.987$$



## Common Emmitter Analysis

### DC Analysis:

$$I_{biase} = \frac{I_c}{5} \Rightarrow I_{biase} = 2\text{m}/5\text{A}$$

$$R_{c1} = \frac{9 - V_c}{I_c} = \frac{9 - 4}{2\text{m}} = 2.5\text{k}\Omega$$

$$R_{E1} = \frac{V_E}{I_c \approx I_E} = 0.1\text{k}\Omega$$

GET  $R_{B1b}$  &  $R_{B1a}$ :

$$V_B = V_{E1} + 0.7 = 1.7\text{ V}$$

$$V_B = 9 \frac{R_{B1a}}{R_{B1b} + R_{B1a}} \Rightarrow \textcircled{1}$$


$$I = \frac{9}{R_{B1b} + R_{B1a}} = 2\text{m}/5 \Rightarrow \textcircled{2}$$

$$R_{B1a} = 4.25\text{k}\Omega$$

$$R_{B1b} = 18.2\text{k}\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{I_C}{26\text{m}} = 0.0769\text{ S}$$
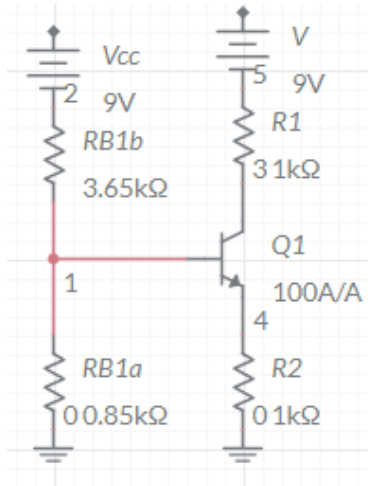
$$r_{\pi} = \frac{\beta}{g_m} = 1300\Omega$$



### AC Analysis:

$$R_{in1} = R_{B1b} // R_{B1a} // R_x$$

$$R_x = \frac{V_{in}}{I_x} = \frac{V_{\pi} + \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) R_e}{\frac{V_{\pi}}{r_{\pi}}}$$

$$= r_{\pi} (1 + g_m R_e)$$

Note that  $R_e$  is a part of  $R_E$ ,

If  $R_e = 0$  ;  $R_{in1} = 943\Omega$

If  $R_e = 500\Omega$  ;  $R_{in1} = 3226.19\Omega$


$$A_{v1} = \frac{V_{out}}{V_{in}} = \frac{-g_m V_{\pi} (R_c // R_{in2})}{V_{\pi} + \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) R_e}$$

$$= \frac{-g_m (R_c // R_{in2})}{1 + g_m R_e}$$

If  $R_e = 0$  ;  $A_{v1} = -140$

If  $R_e = 500\Omega$  ;  $A_{v1} = -3.55$
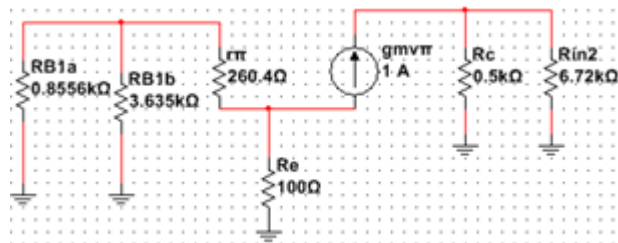
$$R_{out1} = R_c // R_{in2} = 1822\Omega$$



## Over All Gain

$$A_v = \frac{V_{out}}{V_{out1}} \cdot \frac{V_{out1}}{V_{in}} \cdot \frac{V_{in}}{V_{sig}} \cdot 1 = A_{v2} \cdot A_{v1} \cdot \frac{R_{in1}}{R_{in1} + R_{sig}} \cdot 1$$

$$\text{If } R_E = 0 \implies A_v = 0.987 \times 140 \times \frac{943}{943 + 50} = 131.22$$


$$\text{If } R_E = 0.5\text{k}\Omega \implies A_v = 0.987 \times 3.55 \times \frac{3226.19}{3226.19 + 50} = 3.45$$

### 3.A table summarizing the component values

First Stage	Common Emmitter
RB1a	0.85k $\Omega$
RB1b	3.65k $\Omega$
Rc1	0.5k $\Omega$
RE1	0.1k $\Omega$
Rin1	943 $\Omega$ ; If Re =0 ; 3226.19 $\Omega$ ;If Re=500 $\Omega$
Av1	-140; If Re =0 ; -3.55;If Re=500 $\Omega$ ;
Second Stage	Common Collector(Emmitter Follower)
RB2	7.67k $\Omega$
RE2	0.2k $\Omega$
Rin2	6.72k $\Omega$
Av2	0.987
Third Stage	Power Amplifier (Class AB)
RB3a	0.2k $\Omega$
RB3b	0.2k $\Omega$
Rin3	0.1k $\Omega$
Av3	1
Over All Gain	
Av	131.22 If RE =0 3.45 If RE =500 $\Omega$
Rout1	1822 $\Omega$
Rout2	99.58 $\Omega$

## 4. Simulation Results

### 4.a wattmeter reading

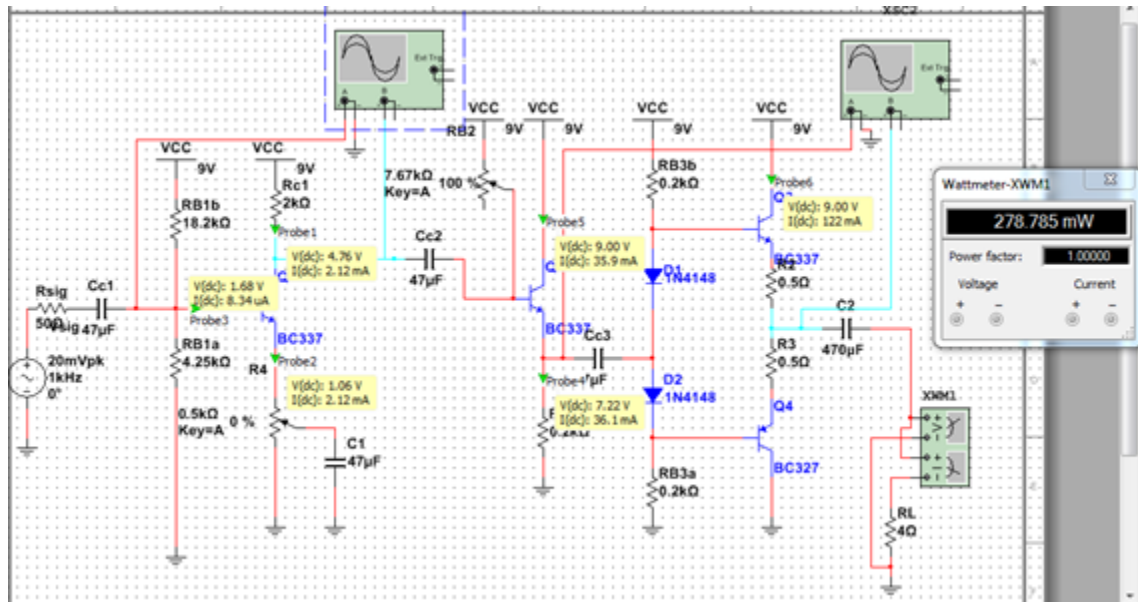


This figure shows the schematic with wattmeter reading.


The wattmeter reading is nearly 278mw which is greater than 250mw.


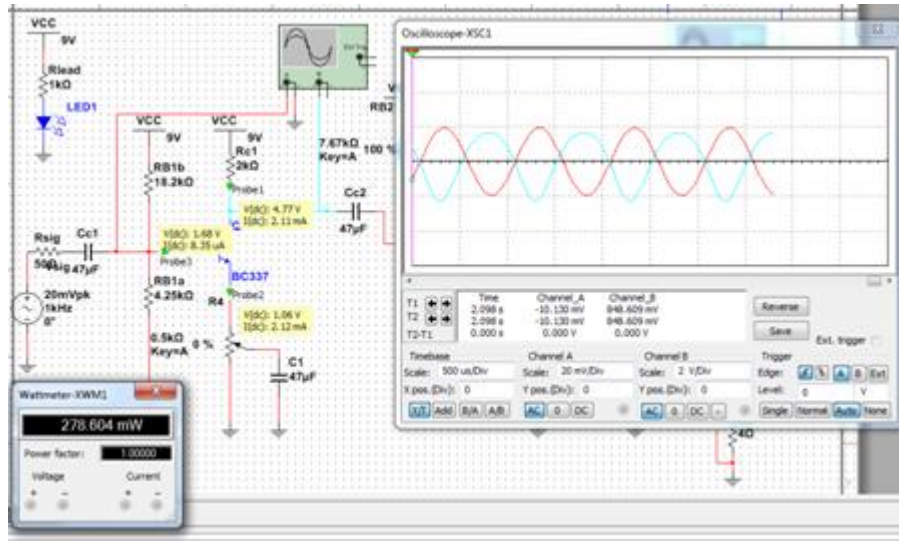
### Output signal of 1<sup>st</sup> stage



Output signal of 2<sup>nd</sup> stage

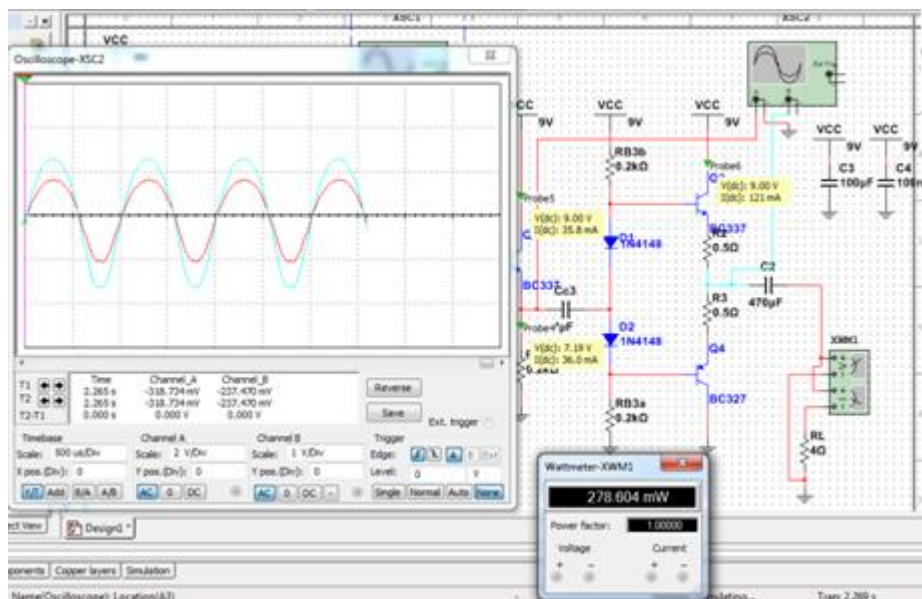

#### 4.c Voltage gain from the simulation

1<sup>ST</sup> stage :

$$Av1 = \frac{\text{channel } B}{\text{channel } A} = \frac{-2.287}{19.14} = -0.123$$


2<sup>nd</sup> stage :

$$Av2 = \frac{\text{channel } B}{\text{channel } A} = \frac{1.266}{1.587} = 0.8$$

#### 5.Comparison between The Voltage Gain Obtained from the simulation & hand result

Stage	Simulation	Hand result
1 <sup>st</sup>	-0.123	-3.55
2 <sup>nd</sup>	0.8	0.98

## 6. Prototype photograph

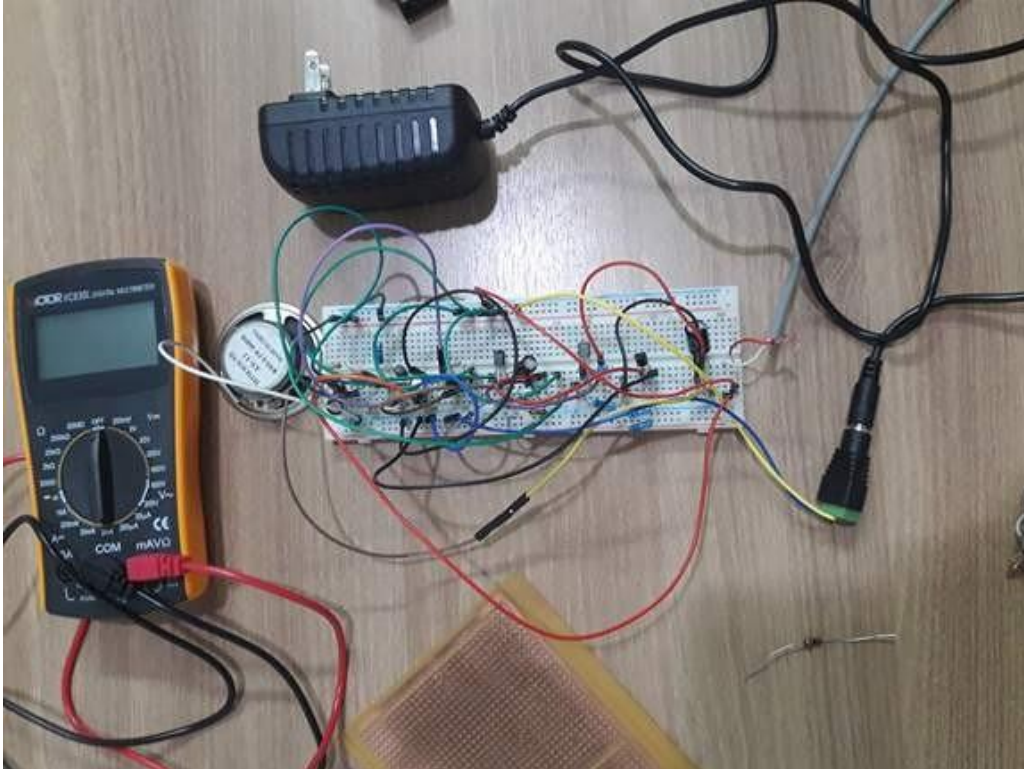


## 7.Maximum and Minimum Frequency

Frequency	Simulation	Circuit
Min	245 HZ Power=139.2885mW	
Nominal	1 KHZ Power=278.577mW	
Max	1205 KHZ Power=139.2mW	
Band width	960 HZ	

## 8. Bonus Project

### Regulated Power Supply

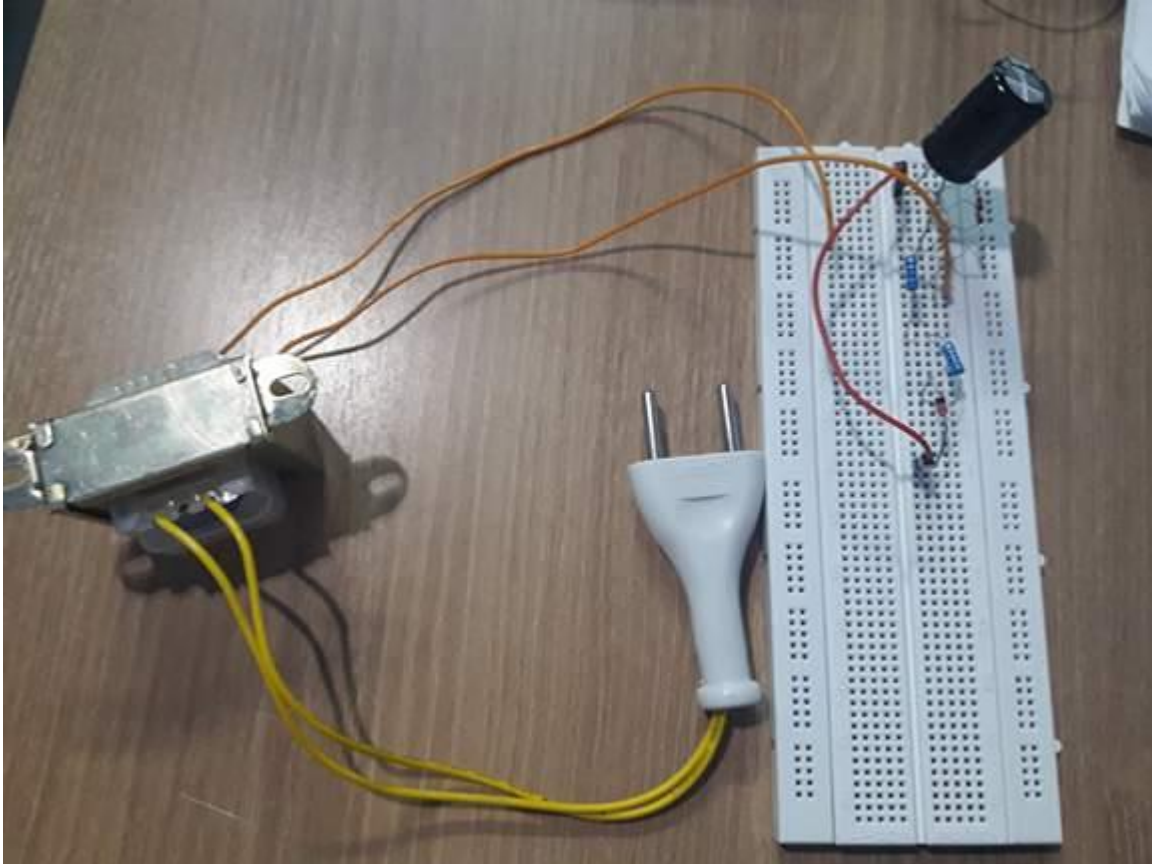

## Analysis of the power supply

From the simulation of the amplifier project:

We get :  $I_L = 178\text{mA}$

From the data sheet of zener diode:

We get :  $I_Z = 150\text{mA}$

$I_{\text{Total}} = I_L + I_Z$

$= 178\text{mA} + 150\text{mA} = 328\text{mA}$

$V_C = V_p - 2V_{\text{deon}}$

$= 12\text{V} - 2 \times 0.8 = 15.37\text{V}$

$I_{\text{Total}} = \frac{V_C - V_Z}{R}$

$R = 19.42\Omega$

